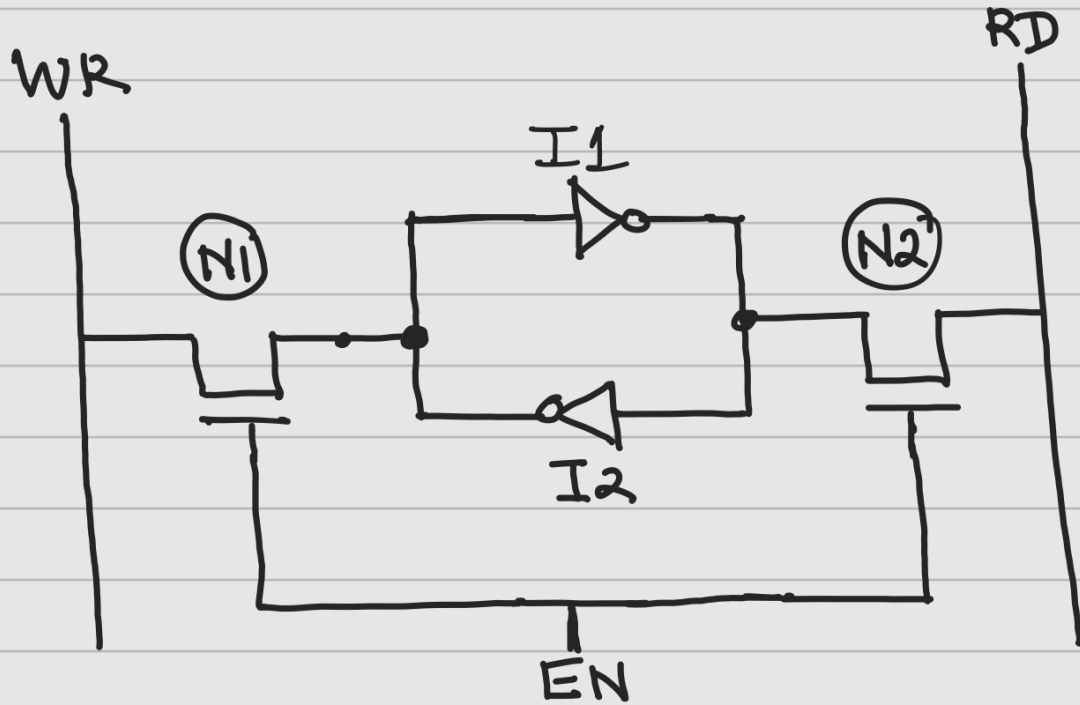


SYMBOL - LEVEL SCHEMATIC ::



I1, I2 : CMOS Inverter's

N1, N2 : NMOS Switches

WR : Write-Line

RD : Read-Line

EN : Write-enable

* Operation :-

Case - 1 :- $EN = 1 \Rightarrow N1 = N2 = ON$

(a) $WR = 1$:

o/p of N1 = W-1

o/p of I1 = S-0

o/p of N2 = RD = S-0

(b) $WR = 0$

o/p of N1 = S-0


o/p of I1 = S-1



o/p of N2 = RD = W-1

Case - 2 :- $EN = 0 \Rightarrow N1 = N2 = OFF$

RD-Line is disconnected from WR-line
 \therefore No CHARGE condition.

⊛ MOSFET-level Schematic:-

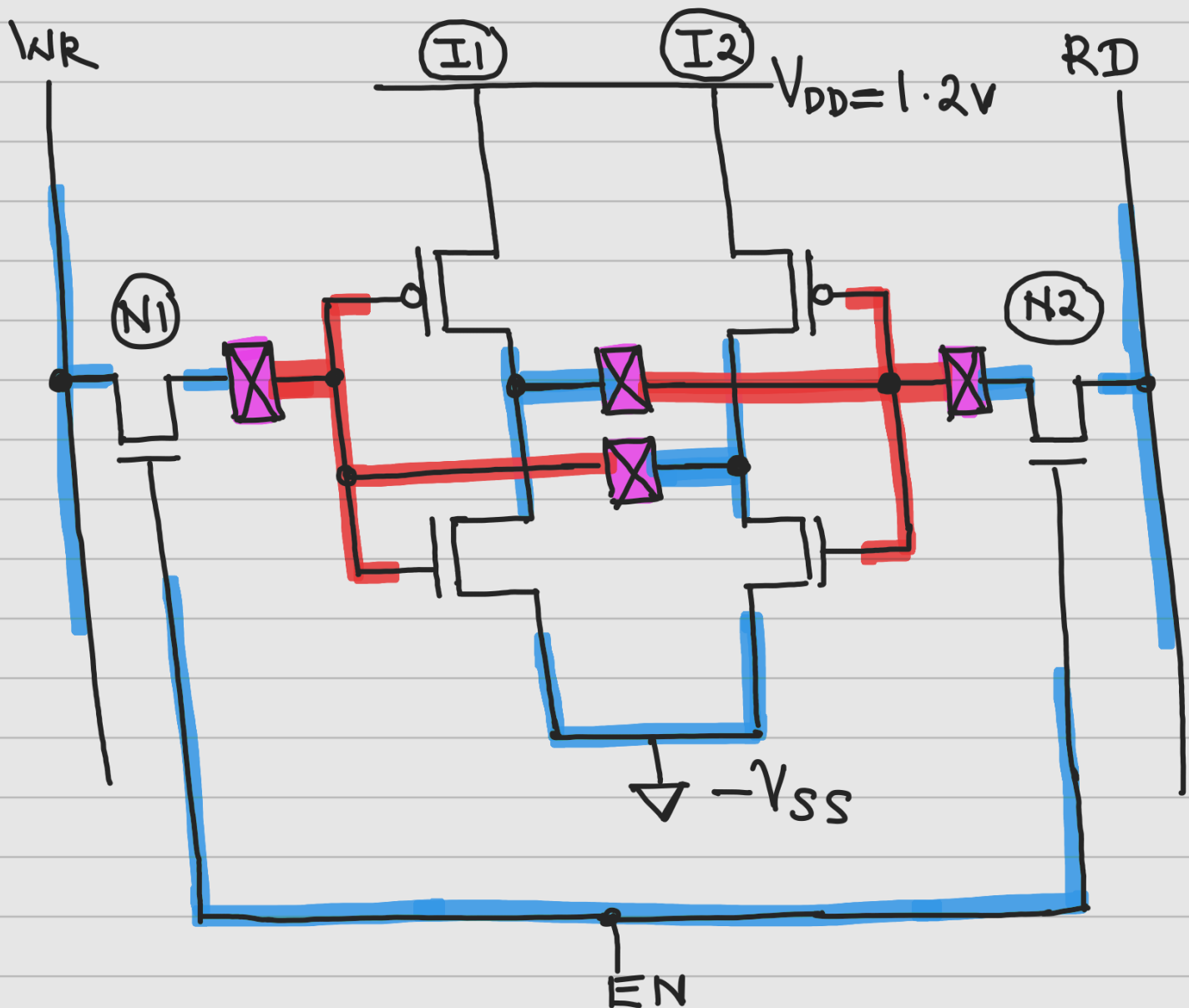

   Metal-1 Layer
 polysilicon Layer

$$(*) \frac{W_p}{L_p} = \left(\frac{500}{100} \right) \text{nm} = 5 = p$$

$$*) \frac{W_N}{L_N} = \left(\frac{500}{100} \right) \text{nm} = 5 = n$$

(*) $\frac{p}{n} = \frac{5}{5} = 1 \Rightarrow \text{Relative size.}$