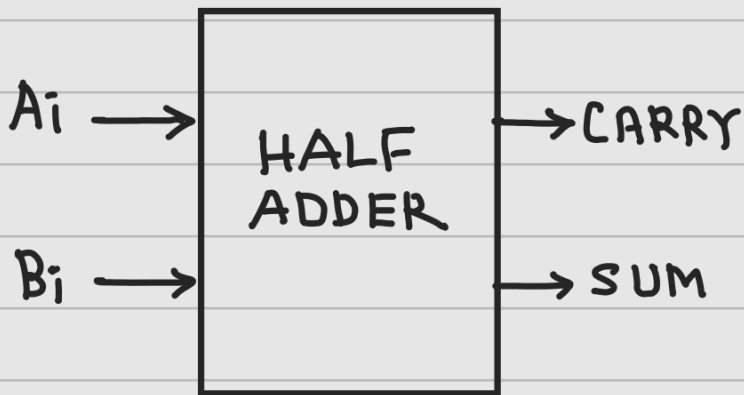


BLOCK DIAGRAM, Truth-Table OF HALF-ADDER

Block Diagram



Truth-Table

A_i	B_i	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$\text{SUM} = A_i \oplus B_i, \text{ CARRY} = A_i \cdot B_i$$

GATE-LEVEL SCHEMATIC OF HALF-ADDER



2:1 MULTIPLEXER SYMBOL & TRUTH-TABLE

SYMBOL

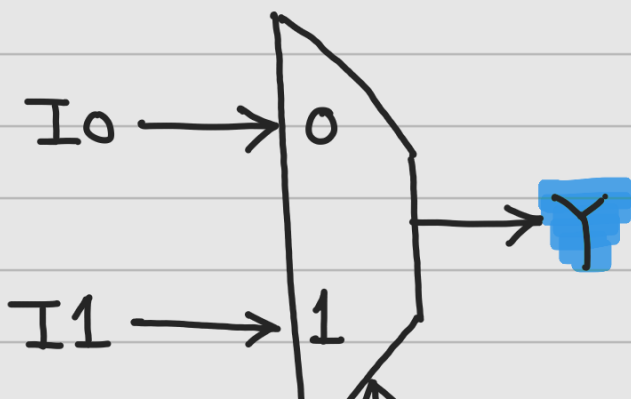

TRUTH-TABLE

S	Y
0	I_0
1	I_1


S

CONVERTING 2:1 Multiplexer into Ex-OR Gate

TRUTH-TABLE OF EX-OR Gate

	A_i	B_i	Y_{xor}	
$A_i = 0$	0	0	0	$Y_{xor} = B_i$
	0	1	1	
$A_i = 1$	1	0	1	$Y_{xor} = \overline{B_i}$
	1	1	0	

\therefore Give A_i as Select line of MUX
 B_i as I_0 i/p of MUX
 $\overline{B_i}$ as I_1 i/p of MUX

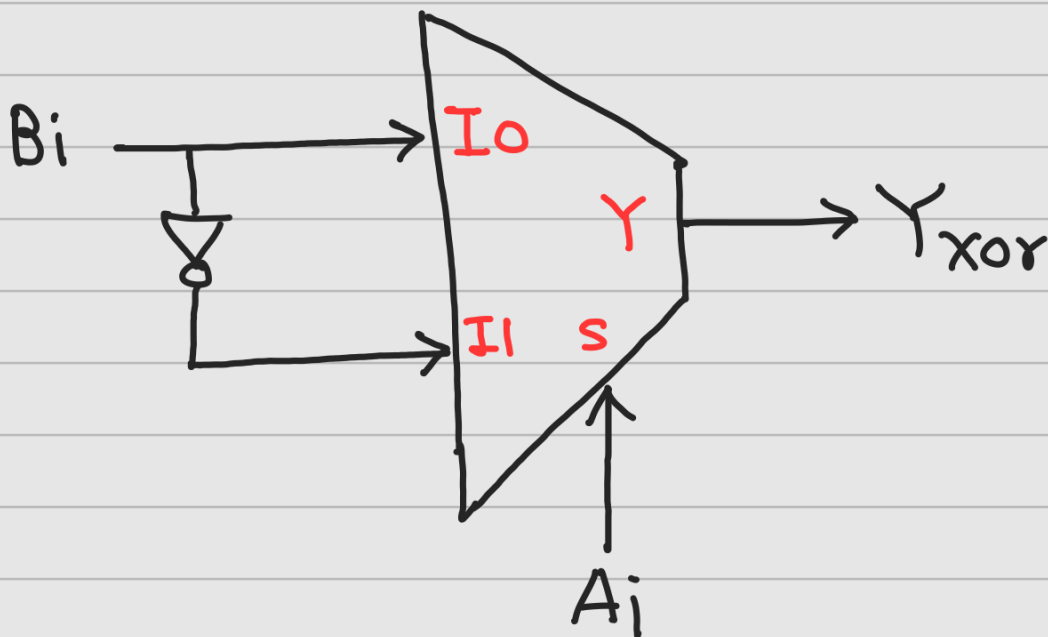


CONVERTING 2:1 Multiplexer into AND Gate


TRUTH-TABLE OF AND Gate

	A_i	B_i	Y_{xor}	
$A_i = 0$	0	0	0	$\} \quad Y_{xor} = 0$
	0	1	0	
$A_i = 1$	1	0	0	$\} \quad Y_{xor} = B_i$
	1	1	1	

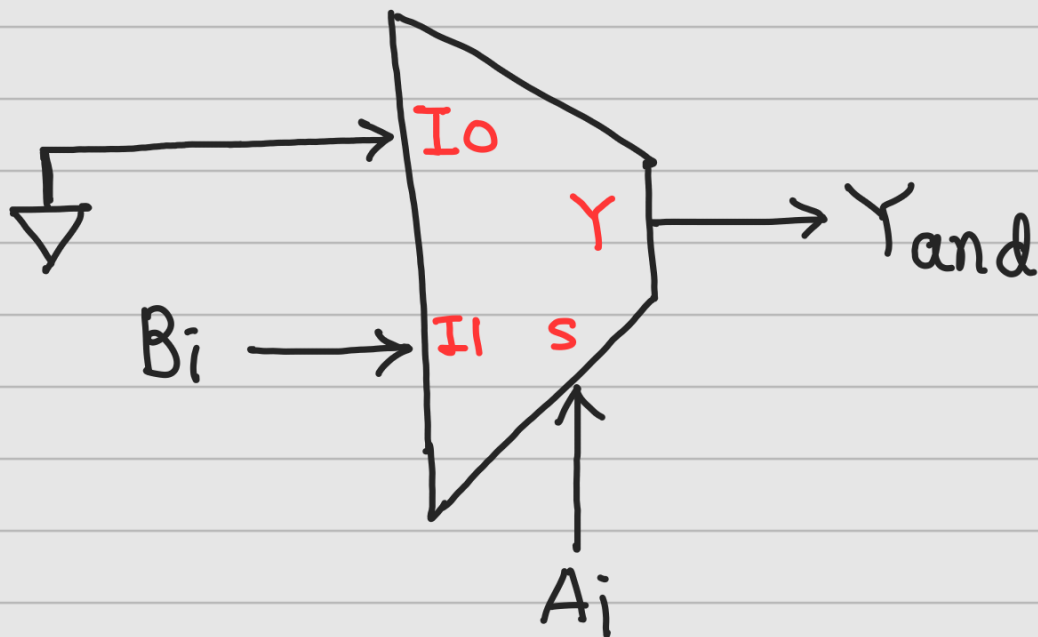\therefore Give A_i as Select line of MUX
 0 as I_0 i/p of MUX
 B_i as I_1 i/p of MUX





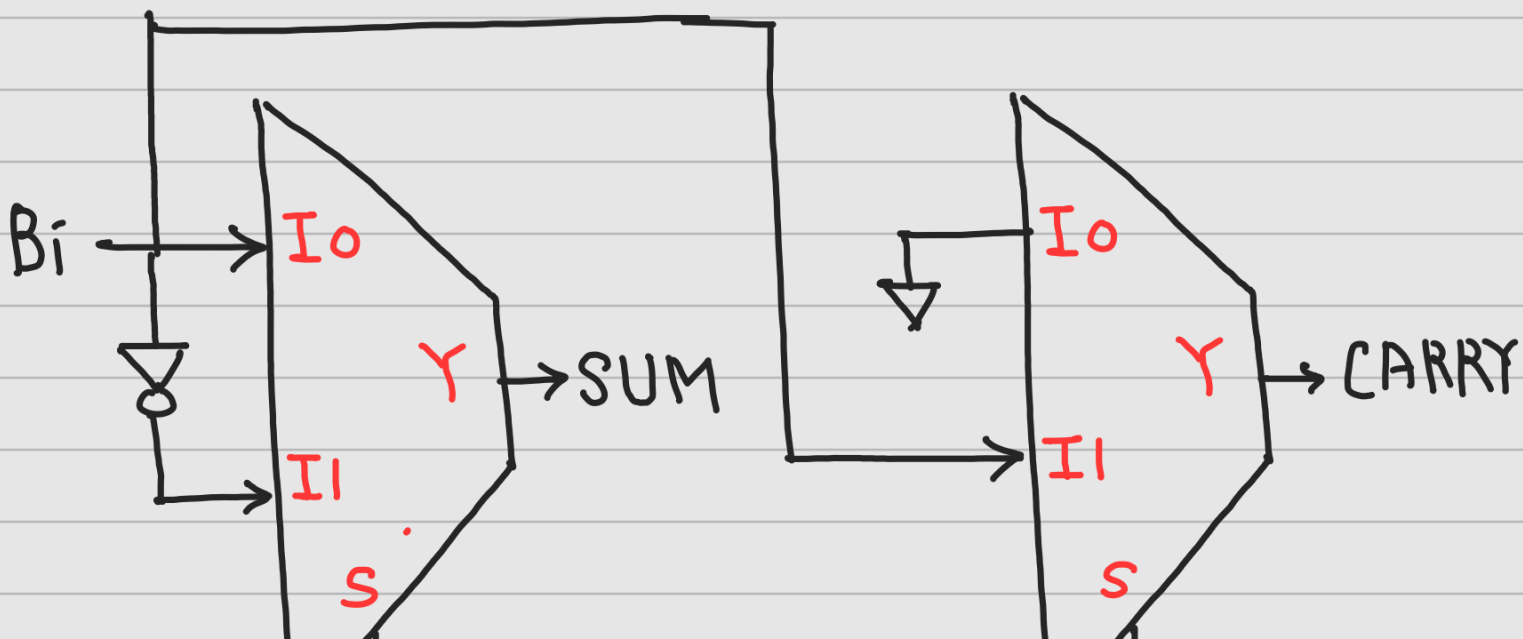MULTIPLEXER Level Schematic of Half-Adder



■ A_i

LAYER CONNECTIONS

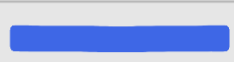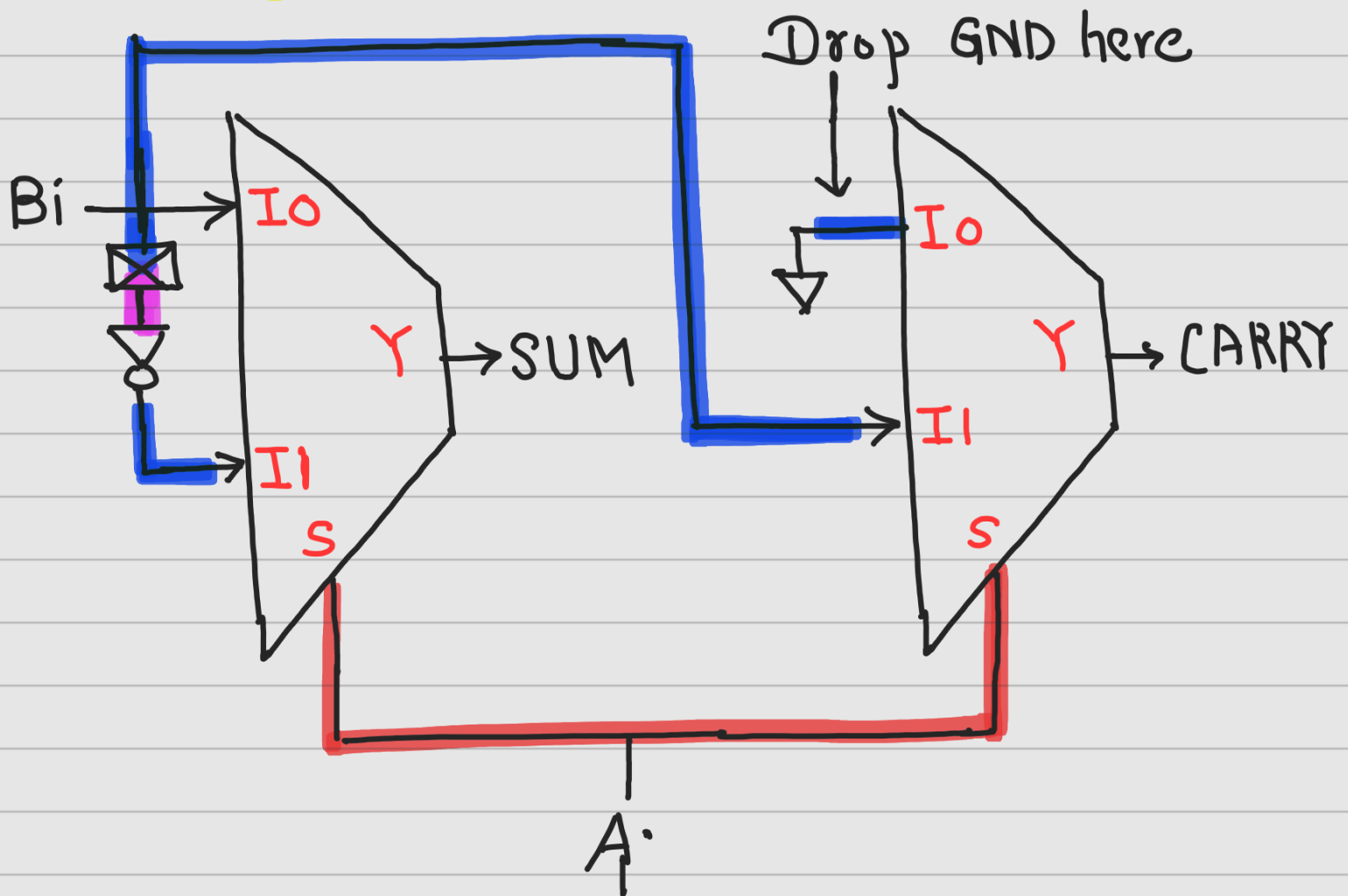

Metal-1 Layer



Polysilicon Layer



Metal-1 To Polysilicon Contact