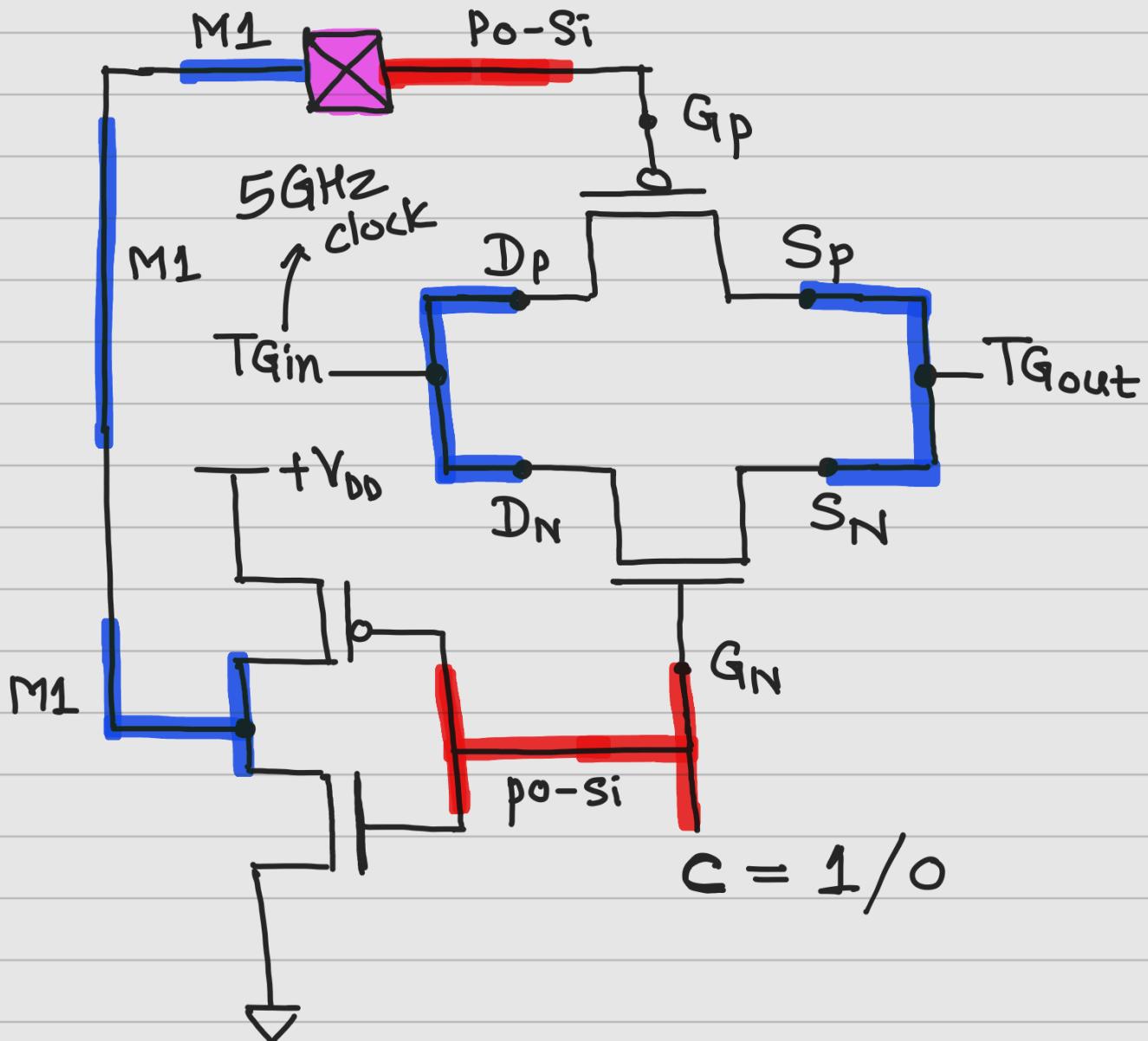


MOSFET- LEVEL SCHEMATIC OF TG



$$\underline{\text{PMOS}}: \frac{W_p}{L_p} = \left(\frac{500}{100}\right) \text{nm} = 5 = p \quad \left\{ \frac{p}{n} = 1 \right.$$

$$\underline{\text{NMOS}}: \frac{W_n}{L_n} = \left(\frac{500}{100}\right) \text{nm} = 5 = n \quad \left. \right\}$$

Metal-1 Layer (M1)
 Polysilicon Layer (Po-Si)

Metal-1 To Polysilicon contact
 closed & S/w

For $C = 1$, $TG_{out} = TG_{in}$ (S-1, S-0)
 $C = 0$, $TG_{out} \neq TG_{in}$ (Open S/w)